

# **A 38.1Mb/mm<sup>2</sup> SRAM in 2nm CMOS Nanosheet Technology for High Density and Energy Efficient Compute Applications**

**Nandini Kumawat**



UNIVERSITY OF MINNESOTA

**Driven to Discover®**



# Outline

- 2nm Technology Highlight
- SRAM Bit Cell and scaling trend
- SRAM design techniques
  - Maximize bit cell array efficiency
  - Far-End (FE) - Write Assist
  - FE-Pre-Charger
  - Double Pump SRAM Design for HPC
- Silicon results
- Summary



 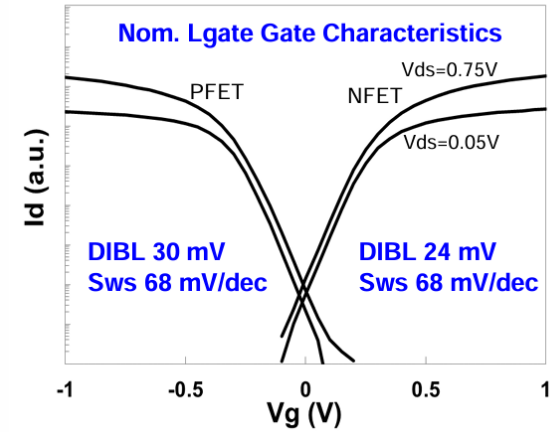
# 2nm Technology Overview

- Successfully transitioned to Nanosheet (NS) era
- Defined and optimized with 3DIC for energy efficiency compute and system integration.
- Energy efficient NS transistors with excellent drives, DIBL and Subthreshold Swing



 
# 2nm Technology Overview



- MEOL/BEOL offers 20% RC reduction and optimized design rules for densest design



# SRAM Bit Cell Scaling Trend

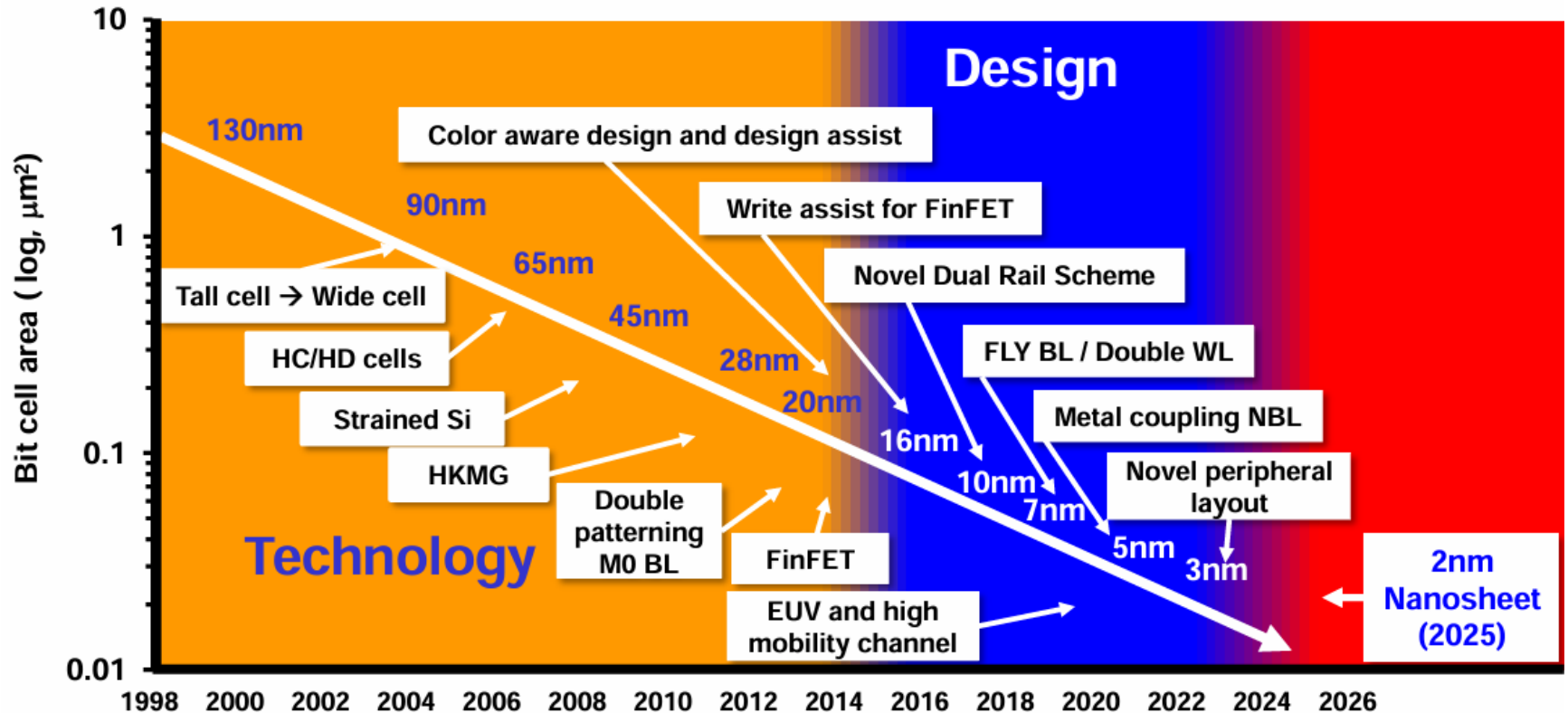


# Peripheral Layout for HD Cell

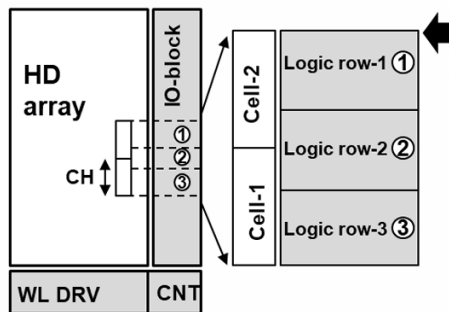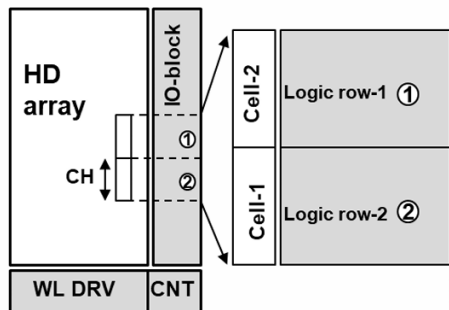

Area  
reduction

Compact  
Peripheral  
Layout

- Cell-area scaling becomes harder at advanced nodes, demanding DTCO.
- Need co-optimization of bitcell and periphery to maintain density improvements.
- 2 nm nanosheets offer higher  $I_{on}/I_{off}$ , allowing longer bitlines without margin loss.
- This work reduces periphery area and increases array utilization.
- Supports up to **2 x larger BL loading** than 3 nm while keeping timing stable.
- Requires special logic design rules to handle increased BL length.

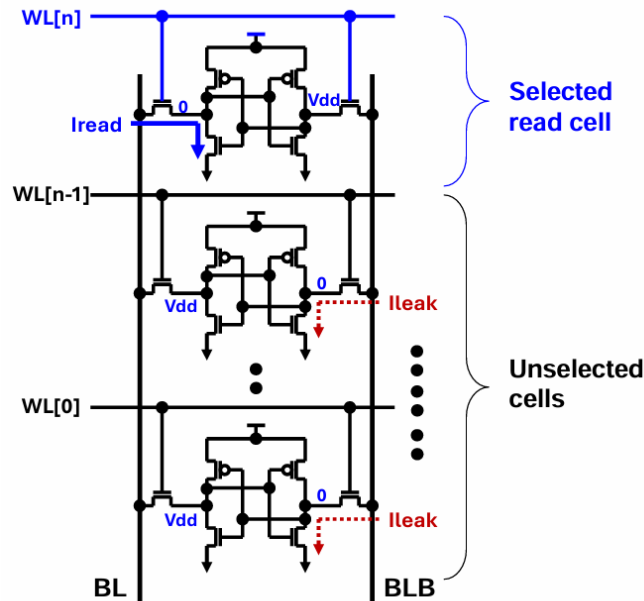


$$SN\ ratio = \frac{I_{on}}{I_{off}} = \frac{I_{read}}{n * I_{leak}}$$

 
# FBL Macro Architecture

- FinFET SRAM limits bitline length to **256 cells per BL** due to weaker Ion/Ioff and higher leakage.
- 2 nm nanosheet SRAM supports **512 cells per BL**.
- Higher Ion improves BL discharge speed, and lower Ioff limits leakage from unselected cells, enabling longer BLs without margin loss.


- Increasing BL capacity to 512 cells boosts **array efficiency**.
- Using **flying bitline (FBL)** routing, the top bank's bitlines connect to the Main IO (MIO) block using Metal-2 over the bottom bank.
- This creates a **1024-row pseudo-BL** structure, improving density and simplifying global routing.



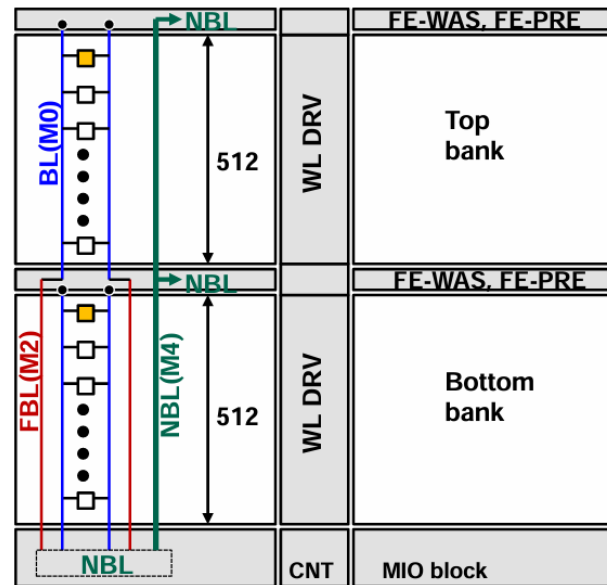SRAM Macro: 580 kb  
 Cell size: 0.021  $\mu\text{m}^2$   
 Density: 38.1 Mb/mm $^2$




# Challenge

 

$$|V_{NBL_{far}}| \ll |V_{NBL_{near}}|$$

# Mitigation

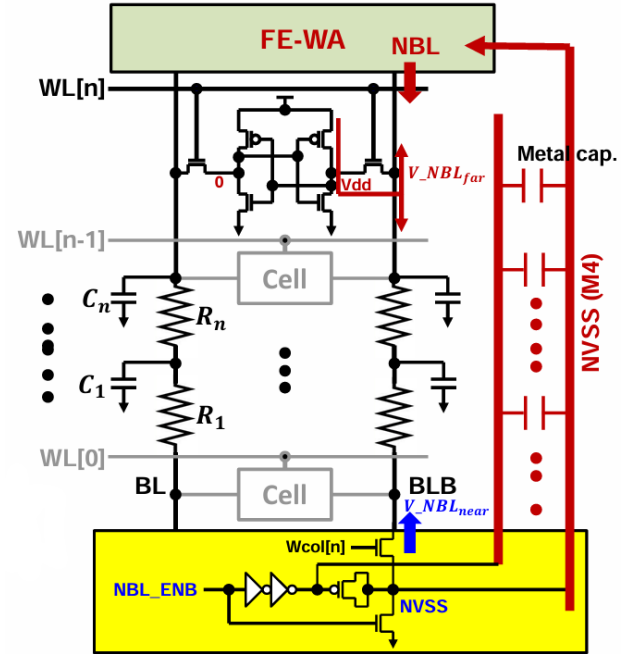


$$|V_{NBL_{far}}| \cong |V_{NBL_{near}}|$$






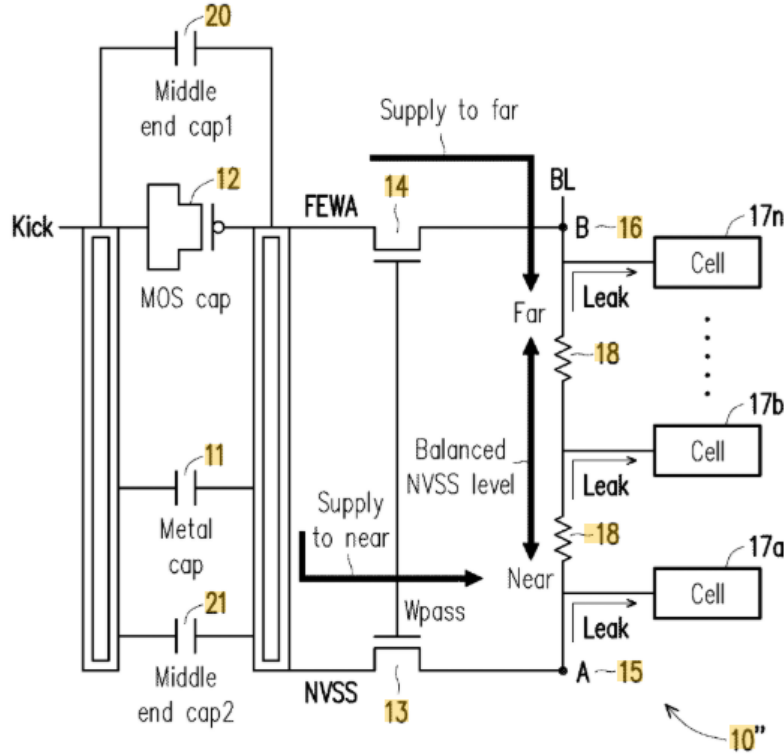
## Balanced Negative Bitline Voltage for a Write Assist Circuit







- You tie a MOS capacitor and a metal capacitor in parallel to boost total capacitance.
- You connect their plates to the bitline through switch transistors at the near end and far end.
- You apply a falling negative kick to the first plates of both capacitors.

**Source:** <https://patents.google.com/patent/US20210201977A1/en>

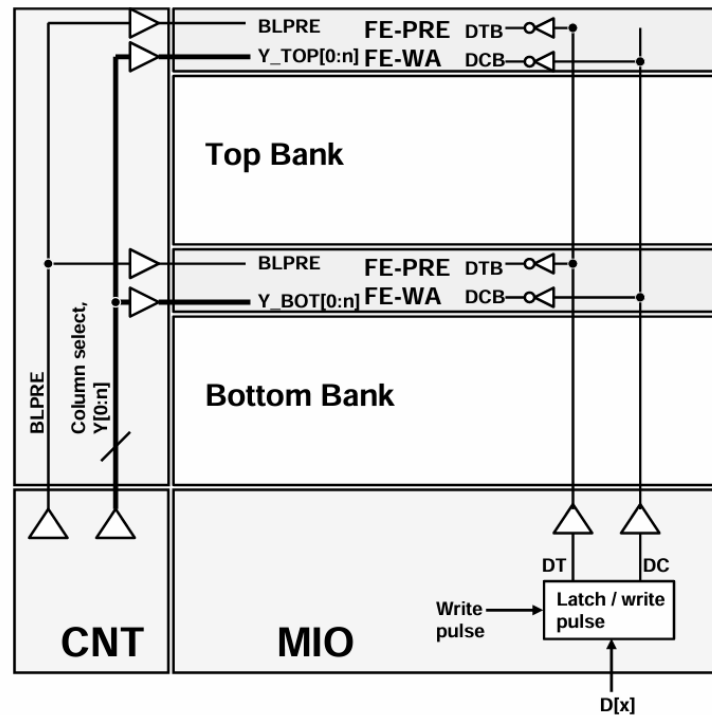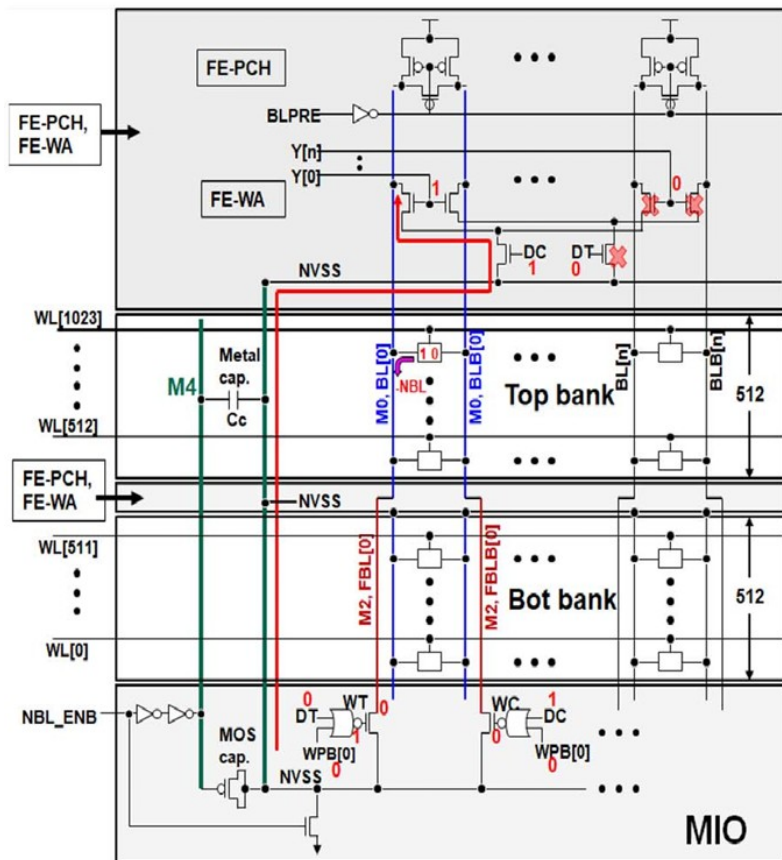
$$V_B = -\frac{C_c}{C_c + C_{par}} \cdot V_{DD}$$



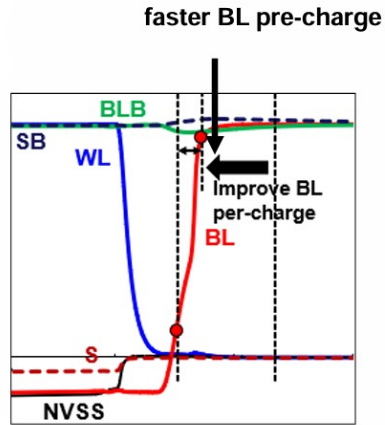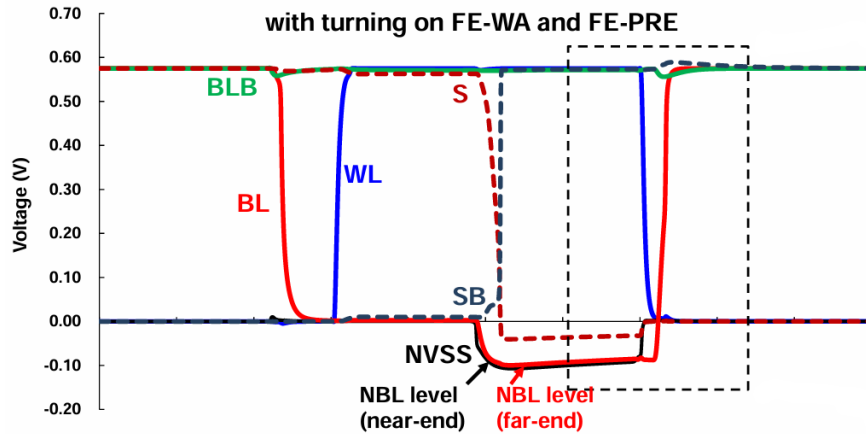 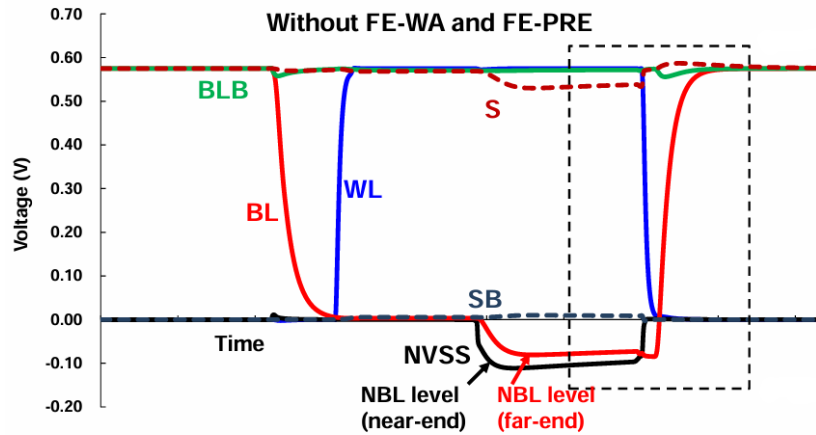
 
# Double-pumped SRAM Design for AI/HPC

- AI/HPC demands high memory bandwidth: Double-pumped 6T SRAM
- Double-pumped SRAM perform 1-Read and 1-Write (1R1W) per cycle
- Better density than 8T (2-Port) SRAM
- Higher BW and  $F_{max}$  than Single-Port SRAM for 1R1W operations





# Dual Tracking Scheme in Double-pumped SRAM

**TURBO ON:** bypass tracking cell to optimize design margin

Fmax: 6.3% improvement while maintaining sufficient RM/WM



Active power: 11.5% reduction, from less BL/BLB swing

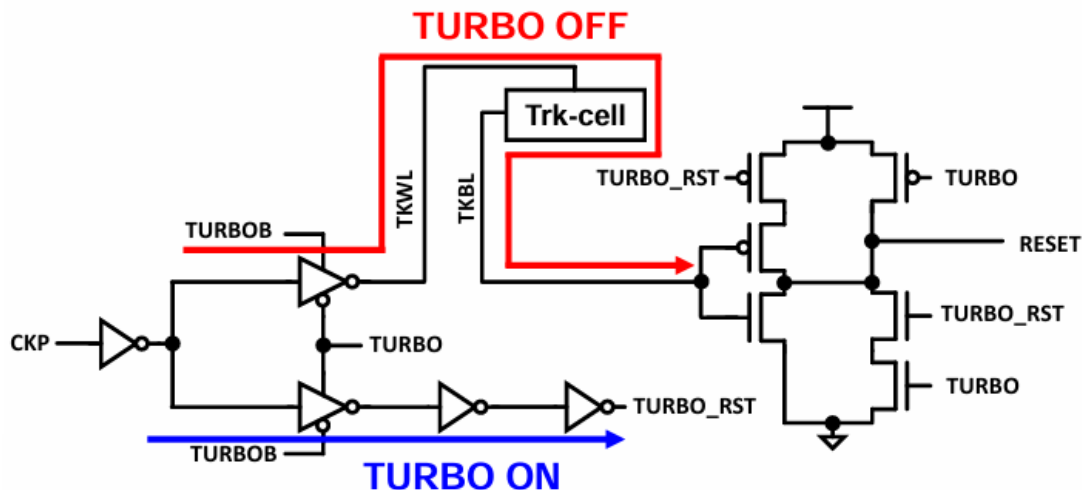 **TURBO OFF:** tracking cell enables lower Vmin operation





# Test Chip

Technology	2nm nanosheet
Metal scheme	1P7M
Supply voltage	0.75V
Bit cell size	HD: $0.021\mu\text{m}^2$
SRAM macro configuration	4096x145 MUX4 (2Mb) 4096x32 MUX16 (256Mb)
SRAM capacity	2Mb and 256Mb
Design Features	Redundancy Programmable E-fuse NBL write assist option

  

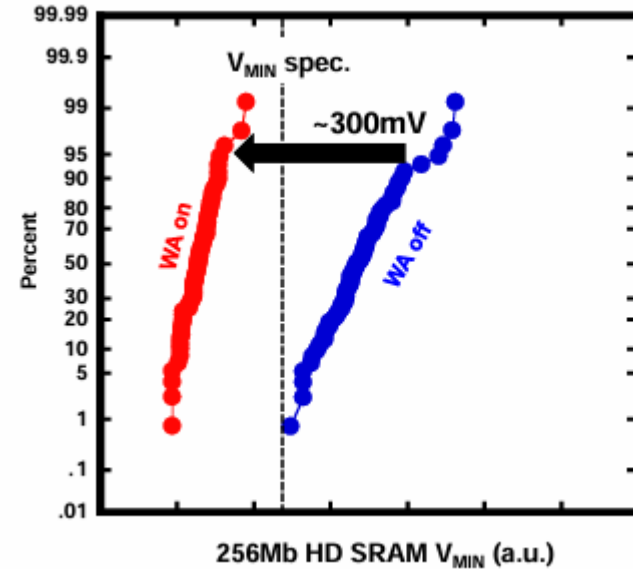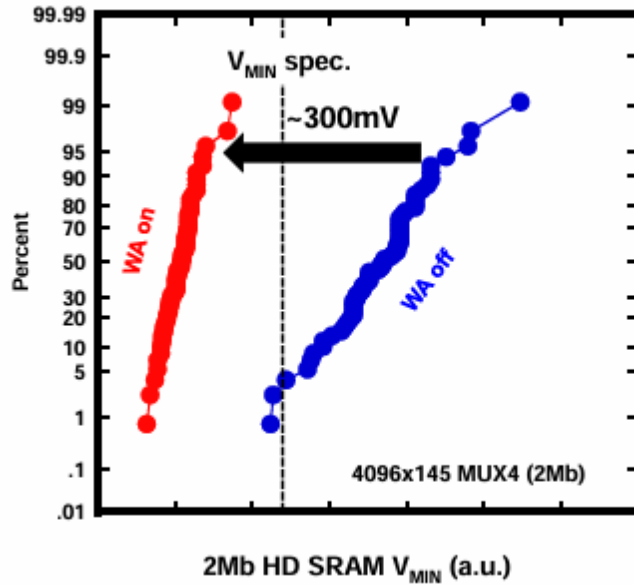
# HD SRAM V<sub>MIN</sub> Cumulative Plot


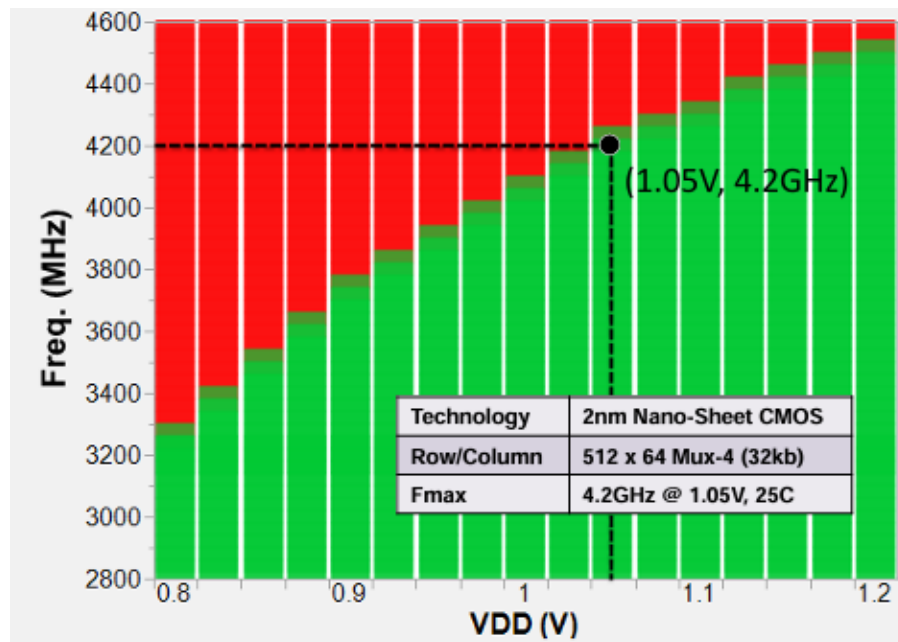
# Fmax Shmoo of Double-Pumped SRAM

Dual-tracking scheme enables  
4.2GHz at 1.05V







UNIVERSITY OF MINNESOTA

**Driven to Discover®**

Crookston Duluth Morris Rochester Twin Cities

The University of Minnesota is an equal opportunity educator and employer.